






# Basic Computer Architecture
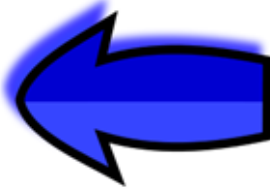
## Chapter 8: Computer Arithmetic (Part I)



# Outline

- \* Addition
  - \* Multiplication
  - \* Division
  - \* Floating Point Addition
  - \* Floating Point Multiplication
  - \* Floating Point Division
- 
- 
- 

# Adding Two 1 bit Numbers

- \* Let us add two 1 bit numbers – **a** and **b**
  - \*  $0 + 0 = 00$
  - \*  $1 + 0 = 01$
  - \*  $0 + 1 = 01$
  - \*  $1 + 1 = 10$
- \* The **lsb** of the result is known, as the **sum**, and the **msb** is known as the **carry**

# Sum and Carry

$$\begin{array}{r} + \quad a \\ \quad b \\ \hline \end{array}$$

carry

sum

$a$	$b$	$s$	$c$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



Truth Table

$$s = a \oplus b = \bar{a}.b + a.\bar{b}$$

$$c = a.b$$
  
# Half Adder

- \* Adds two 1 bit numbers to produce a 2 bit result



# Full Adder



Add **three** 1 bit numbers to produce a 2 bit output

$$a + b + c_{in} = 2 * c_{out} + s$$

a	b	c <sub>in</sub>	s	c <sub>out</sub>
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

*S = 1 if  
Odd number of  
1s is present  
in the i/p*

  *c<sub>in</sub> = 1  
c<sub>out</sub> = 1*



$$S = \bar{a} b \bar{c}_{in} + a \bar{b} \bar{c}_{in} + \bar{a} \bar{b} c_{in} + a b c_{in}$$



S=1 if odd no of 1s in a, b, c<sub>in</sub>

# Equations for the Full Adder


$$\begin{aligned} s &= a \oplus b \oplus c_{in} \\ &= (a \cdot \bar{b} + \bar{a} \cdot b) \oplus c_{in} \\ &= (a \cdot \bar{b} + \bar{a} \cdot b) \cdot \overline{c_{in}} + \overline{a \cdot \bar{b} + \bar{a} \cdot b} \cdot c_{in} \\ &= a \cdot \bar{b} \cdot \overline{c_{in}} + \bar{a} \cdot b \cdot \overline{c_{in}} + \overline{(a \cdot \bar{b}) \cdot (\bar{a} \cdot b)} \cdot c_{in} \\ &= a \cdot \bar{b} \cdot \overline{c_{in}} + \bar{a} \cdot b \cdot \overline{c_{in}} + (\bar{a} + b) \cdot (a + \bar{b}) \cdot c_{in} \\ &= a \cdot \bar{b} \cdot \overline{c_{in}} + \bar{a} \cdot b \cdot \overline{c_{in}} + \bar{a} \cdot \bar{b} \cdot c_{in} + a \cdot b \cdot c_{in} \end{aligned}$$

$$c_{out} = \underbrace{a \cdot b} + \underbrace{a \cdot c_{in}} + \underbrace{b \cdot c_{in}}$$

# Circuit for the Full Adder

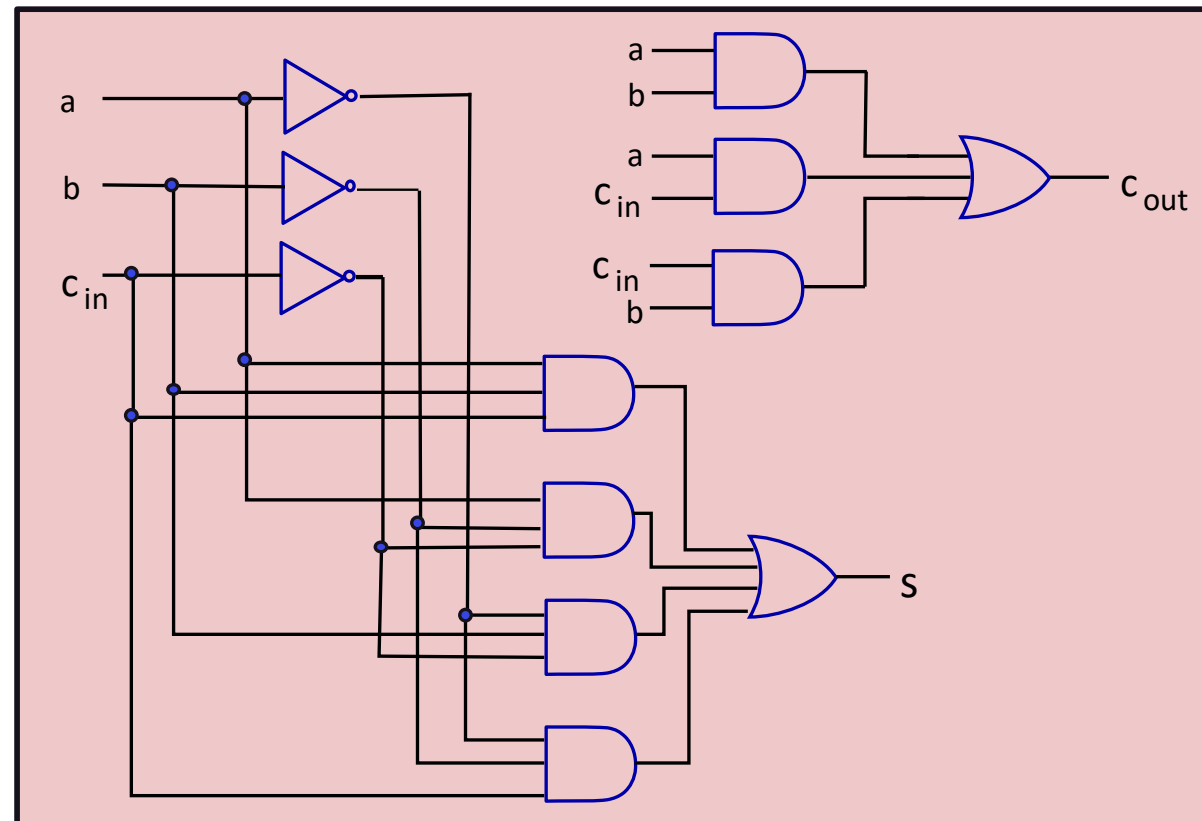 

# Addition of two $n$ bit numbers

 

$$\begin{array}{r} \begin{array}{cccc} \boxed{1} & \boxed{1} & \boxed{1} & \boxed{1} \\ \downarrow & \downarrow & \downarrow & \downarrow \end{array} \\ + \begin{array}{r} 1011 \\ 0101 \\ \hline 10000 \end{array} \end{array}$$

- \* We start from the **lsb**
- \* Add the corresponding pair of bits and the **carry in**
- \* Produce a **sum bit** and a **carry out**

# Observations

- \* We keep adding pairs of bits, and proceed from the lsb to the msb
- \* If a carry is generated, we add it to the next pair of bits
- \* At the last step, if a carry is generated, then it becomes the msb of the result
- \* The carry effectively ripples through the bits


# Ripple Carry Adder

c → carry

Full adder

Half adder

 $t_w$   
 $t_f$   
 $(n-1)t_f + t_n$   
 $= O(n)$



# Operation of the Ripple Carry Adder

- \* **Problem : Add A + B**
- \* Number the bits :  $A_1$  to  $A_n$  and  $B_1$  to  $B_n$ 
  - \* **lsb**  $\rightarrow A_1$  and  $B_1$
  - \* **msb**  $\rightarrow A_n$  and  $B_n$
- \* Use a **half adder** to add  $A_1$  and  $B_1$
- \* Send the carry(c) to a **full adder** that adds :  
 $A_2 + B_2 + c$
- \* Proceed in a similar manner **till the msb**

# How long does the Ripple Carry Adder take ?

- \* Time :
  - \* Time of half adder :  $t_h$
  - \* Time of full adder :  $t_f$
  - \* Total Time :  $t_h + (n-1)t_f$

# Asymptotic Time Complexity

- \* Most of the time, we are primarily interested in the **order of the function**
- \* For example : we are only interested in the  $n^2$  term in  $(2n^2 + 3n + 4)$
- \* We do not care about the **constants**, and terms with **smaller exponents**
  - \*  $3n$  and  $4$
- \* We can thus say that :
  - \*  $2n^2 + 3n + 4$  is order of  $(n^2)$

# The O notation

- \* Formally :
  - \* We say that:  $f(n) = O(g(n))$
  - \* if,  $|f(n)| \leq c|g(n)|$ , for all  $n > n_0$ . Here  $c$  is a positive constant.
- \* In simple terms:
  - \* Beyond a certain  $n$  ,  $g(n)$  is greater-than-equal to a certain constant times  $f(n)$ 
    - \* *For example, beyond 15,  $(n^2 + 10n + 16) \leq 2n^2$*


# Example of the big O Notation

$f(n) = 3n^2 + 2n + 3$ . Find its asymptotic time complexity.

**Answer:**

$$\begin{aligned} f(n) &= 3n^2 + 2n + 3 \\ &\leq 3n^2 + 2n^2 + 3n^2 \quad (n > 1) \\ &\leq 8(n^2) \end{aligned}$$

Hence,  $f(n) = O(n^2)$ .

 

$8n^2$  is a strict upper bound on  $f(n)$  as shown in the figure.

# Big O Notation - II



**Example:**

$f(n) = 0.00001n^{100} + 10000n^{99} + 234344$ . Find its asymptotic time complexity.

**Answer:**  $f(n) = O(n^{100})$

- \* We shall use the asymptotic time complexity metric (big O notation) to characterize the **time taken by different**

**adders**

  

# Ripple Carry Adders and Beyond



\* Time complexity of a ripple carry adder :

\*  $O(n)$

Step 2  
 $O(k)$   
Step 2  
 $O\left(\frac{n}{k}\right)$




\* Can we do better than  $O(n)$  ?

  
 
# Carry Select Adder $O(\sqrt{n})$ time

- \* Group bits into blocks of size (k)
- \* If we are adding two 32 bit numbers A and B, and  $k = 4$ , then the blocks are :



- \* Produce the result of each block with a **small ripple carry adder**

# Carry Select Adder - II

- \* In this case, the **carry propagates across blocks**
- \* Time complexity is  $O(n)$



Idea :

- \* Add the numbers in each block in parallel
- \* Stage I : For each **block**, produce **two results**
  - \* Assuming an **input carry of 0**
  - \* Assuming an **input carry of 1**

# Carry Select Adder – Stage II

- \* For each block we have two results available
- \* Result  $\rightarrow$  (k **sum** bits), and 1 **carry out** bit
- \* Stage II
  - \* Start at the **least significant block**
    - \* The input carry is 0
    - \* Choose the appropriate result from stage I
  - \* We now know the input carry for the second block
    - \* Choose the appropriate result
    - \* Result contains the input carry for the third block

# Carry Select Adder – Stage II

- \* Given the result of the second block
  - \* Compute the carry in for the third block
  - \* Choose the appropriate result
- \* Proceed till the last block
- \* At the last block (most significant positions)
  - \* Choose the correct result
  - \* The carry out value, is equal to the carry out of the entire computation.

# How much time did we take ?

- \* Our block size is  $k$ 
  - \* Stage I takes  $k$  units of time
- \* There are  $n/k$  blocks
  - \* Stage II takes  $(n/k)$  units of time

\* Total time :  $(k + n/k)$

$\rightarrow O(\sqrt{n})$

$$\left| \frac{\partial (k + n/k)}{\partial k} = 0 \right.$$
$$\Rightarrow 1 - \frac{n}{k^2} = 0$$
$$\Rightarrow k = \sqrt{n}$$

# Time Complexity of the Carry Select Adder

- \*  $T = O(\sqrt{n} + \sqrt{n}) = O(\sqrt{n})$
- \* Thus, we have a  $\sqrt{n}$  time adder



Can we do better ?

